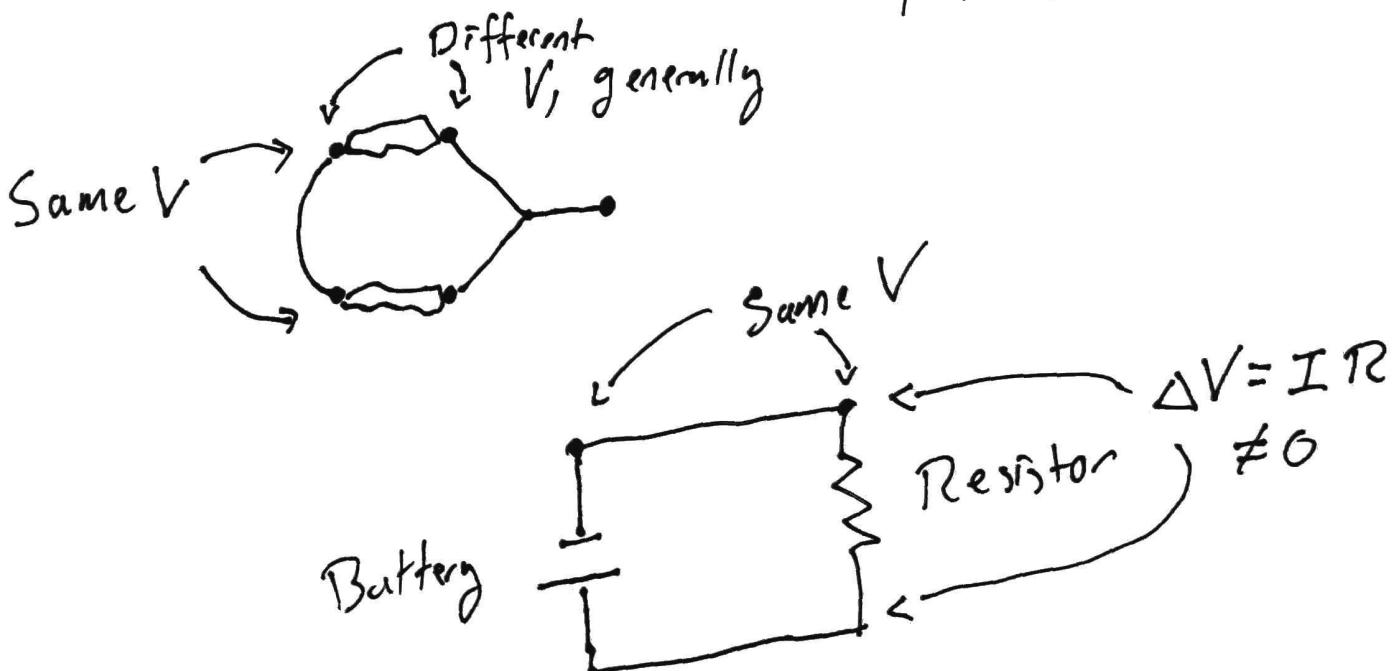


DC Circuits - Resistors and Batteries

Steady state, "lumped element" approximation
(RC Circuits are not steady)


The diagram shows a network of wires connecting various elements. A battery symbol is shown with a wavy line across it, labeled β . Labels include "Wires (Perfect conductors)" pointing to the lines, "Elements" pointing to a central junction, and "B, R, ~~C~~, ..." below the network.

"0th Rule": Two points connected by a wire are at the same potential:



Kirchoff's Laws — Conservation laws for circuits

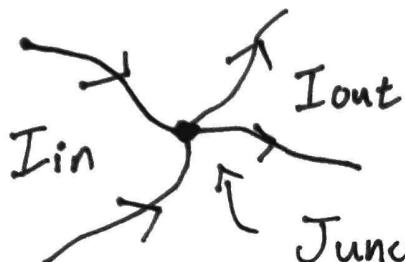
1. "Junction rule" / (conservation of charge)



$$\boxed{\sum I_{in} = \sum I_{out}}$$

Junction - multiple wires attached at a point

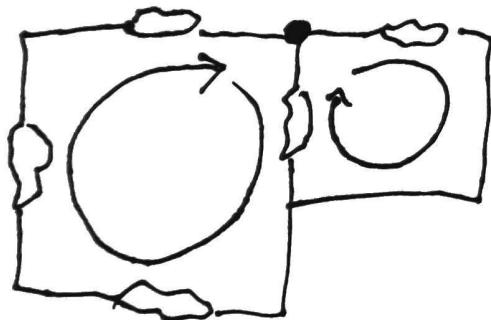2. "Loop rule" / (conservation of energy,
Electric potential is well-defined)



Loop: Directed path along some part of a circuit that ends where it starts

$$\hookrightarrow V_{start} = V_{end}$$

$$\Rightarrow \boxed{\sum_{\text{elements in loop}} \Delta V = 0}$$

$$V_{high} - V_{low}$$



$$V = I \bar{R}$$

$$\text{High } \xleftarrow{\Delta V = E} \text{Low}$$

Basic elements: Battery

Resistor

11

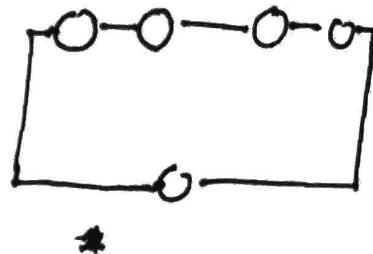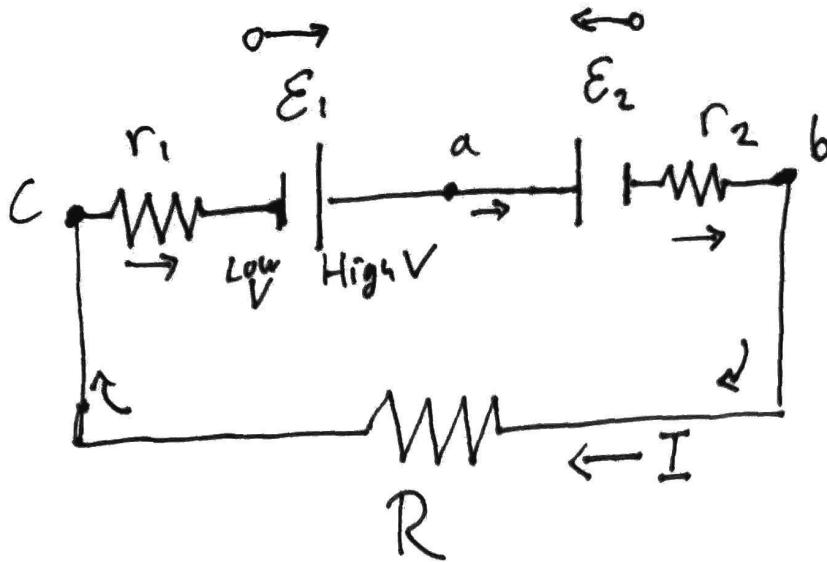

(a) Constant current I , because no branches.

All junctions are like: $\xrightarrow{I_{in}} \textcircled{O} \xrightarrow{I_{out}}$ \textcircled{O} $\xrightarrow{\text{1st Law}}$


Batteries: $+E_1, -E_2$

Resistors: $-Ir_2, -IR, -Ir_1$



2nd Law / Loop rule: $E_1 - E_2 - I(r_2 + R + r_1) = 0$

Solve for I : $I = \frac{E_1 - E_2}{r_1 + r_2 + R}$


(b) Alternatively:

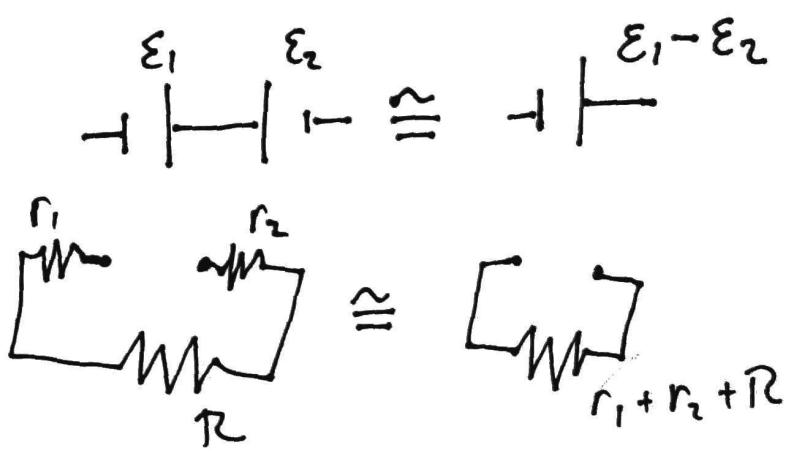

(c) Plot of potential along loop:

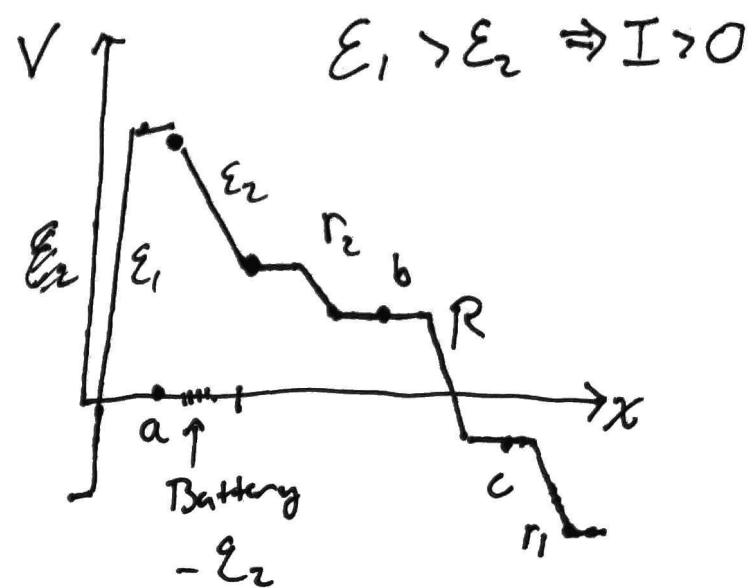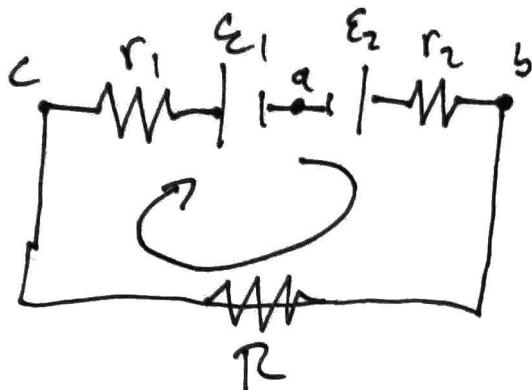


3]

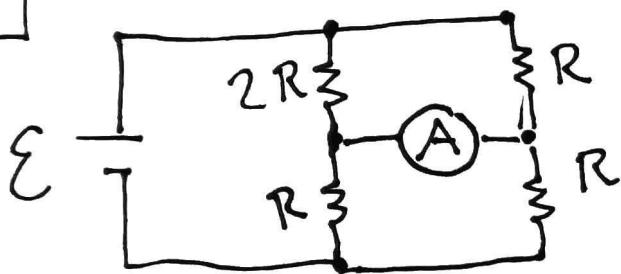



SII

In terms of E , R
want to find the current
flowing through (A)

(A has 0 resistance)

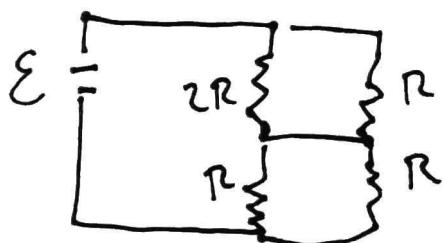


• First, assign current directions.

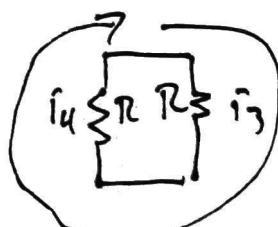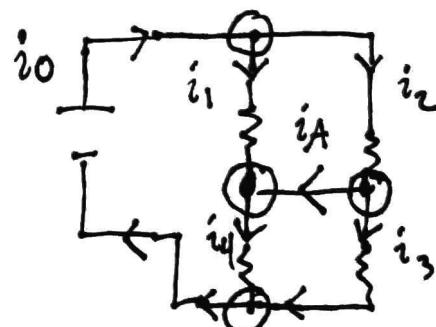

$$-R i_3 + R i_4 = 0$$

$$i_4 - i_3 = 0$$



3]

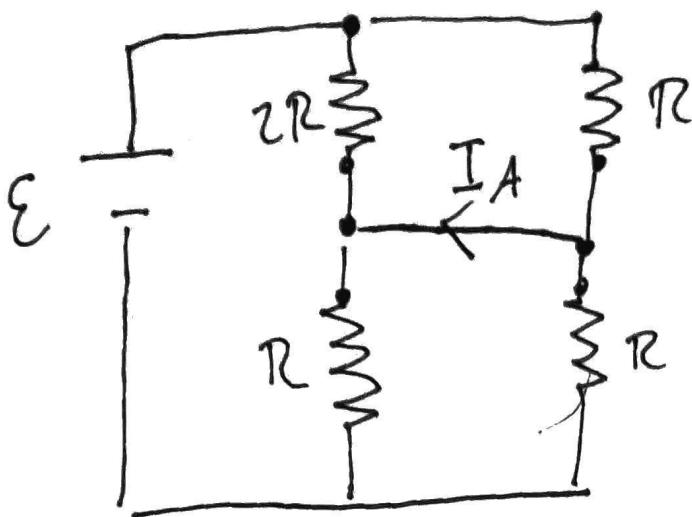


Goal: Find I_A , given
 E, R


Could apply Kirchoff's laws.
(3 loops, 6 junctions...)

Trick:

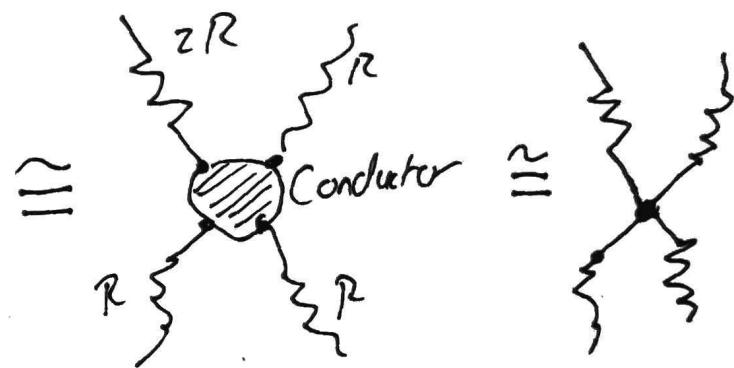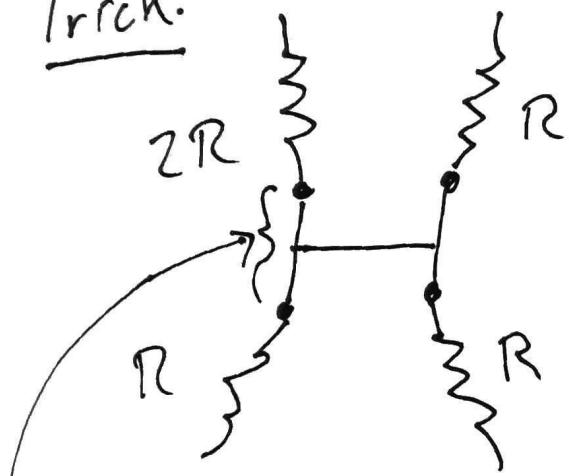

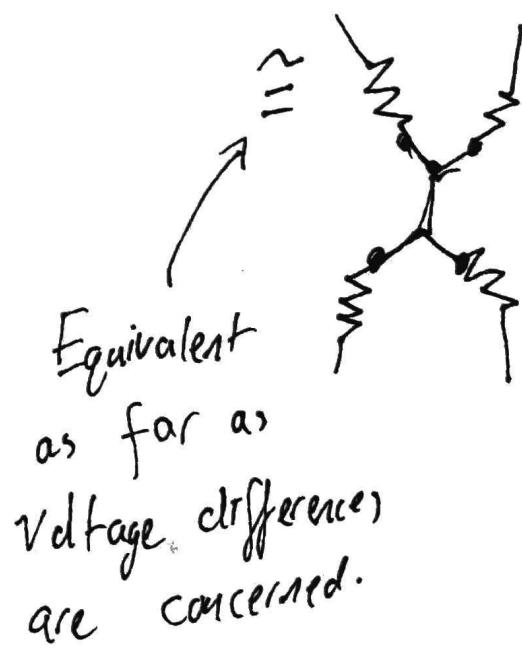Because connected by
ideal wires, everything
in this region is at
same potential.




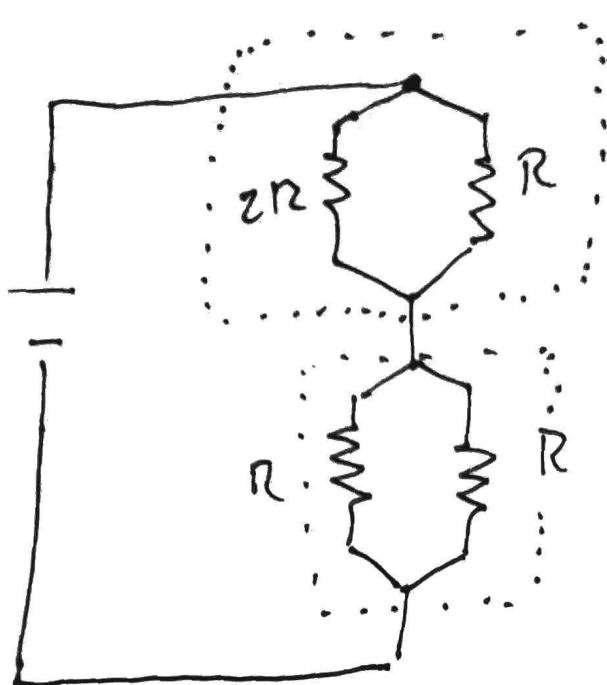


Parallel:

$$R_1 = \left(\frac{1}{2R} + \frac{1}{R} \right)^{-1} = \frac{2}{3} R$$
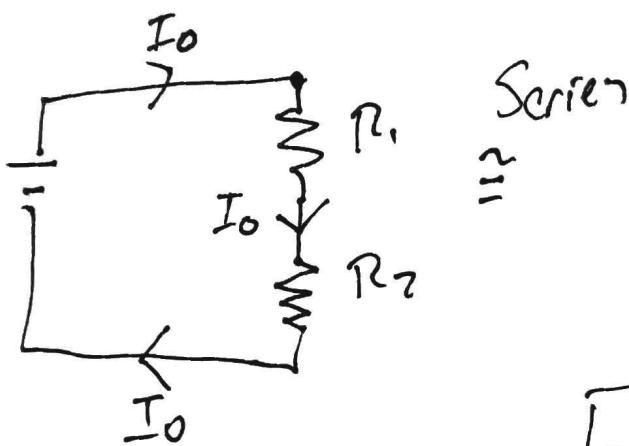
$$R_2 = \left(\frac{1}{R} + \frac{1}{R} \right)^{-1} = \frac{1}{2} R$$



\approx Series

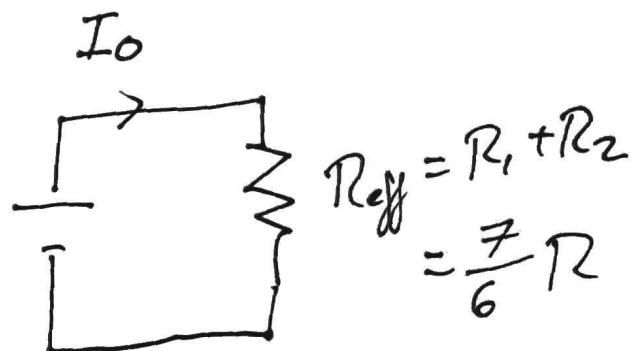


$$\begin{aligned} R_{\text{eff}} &= R_1 + R_2 \\ &= \frac{7}{6} R \end{aligned}$$

$$\boxed{I_0 = \frac{\mathcal{E}}{R_{\text{eff}}} = \frac{6}{7} \frac{\mathcal{E}}{R}}$$

$$\hookrightarrow V_1 = I_0 R_1 = \frac{6}{7} \frac{\mathcal{E}}{R} \cdot \frac{2}{3} R = \frac{4}{7} \mathcal{E}$$

$$V_2 = I_0 R_2 = \frac{6}{7} \frac{\mathcal{E}}{R} \cdot \frac{1}{2} R = \frac{3}{7} \mathcal{E}$$

• Right loop:

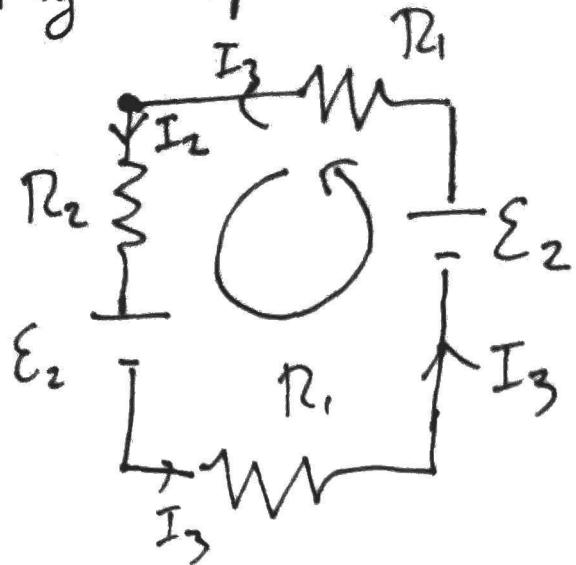

$$0 = -I_2 R_2 - \epsilon_2$$

$$-I_3 R_1 + \epsilon_2 - I_3 R_1$$

$$= -I_2 R_2 - 2 I_3 R_1$$

$$= -I_2 (4\Omega) - 2 I_3 (2\Omega)$$

$$\Rightarrow 0 = -(I_2 + I_3)$$




$$\Rightarrow I_2 = -I_3 \quad (\text{Right loop})$$

$$I_1 - I_2 = 1 \text{ A} \quad (\text{Left loop})$$

$$I_1 + I_2 = I_3$$

$$I_2 = -I_3 = -(2I_2 + 1) \Rightarrow \boxed{I_2 = -\frac{1}{3}} \text{ A}$$
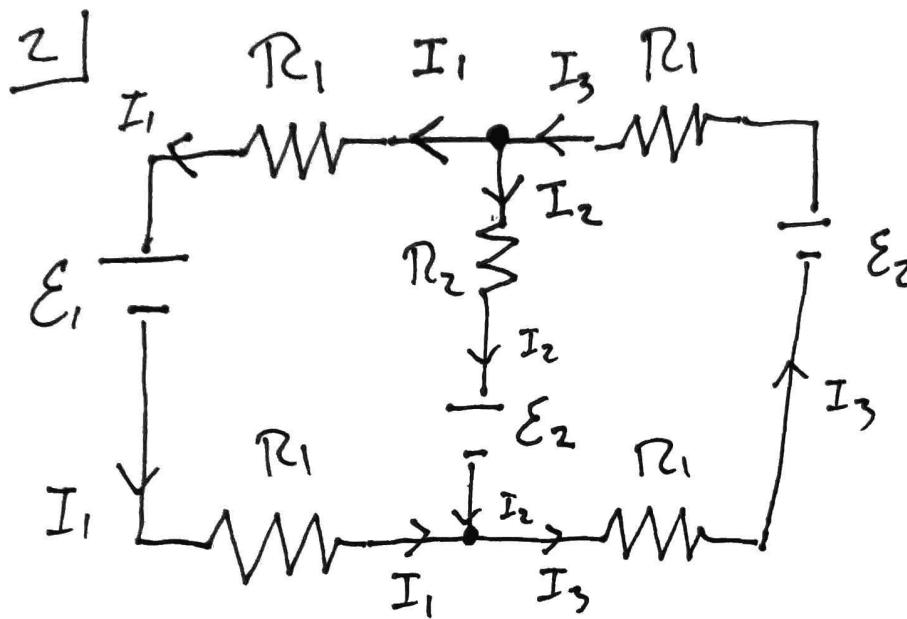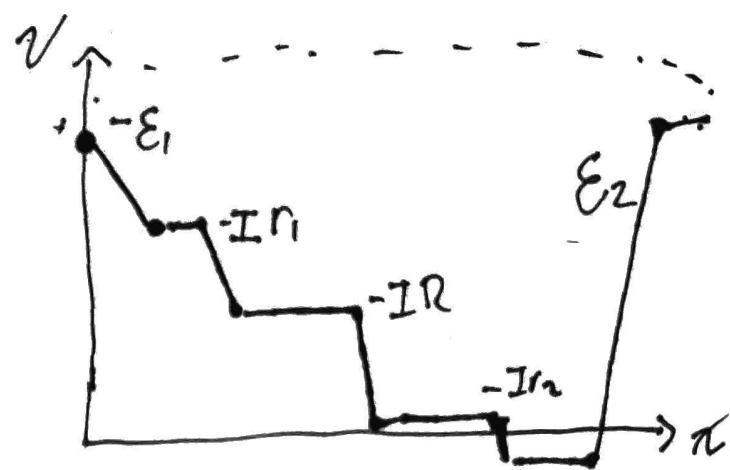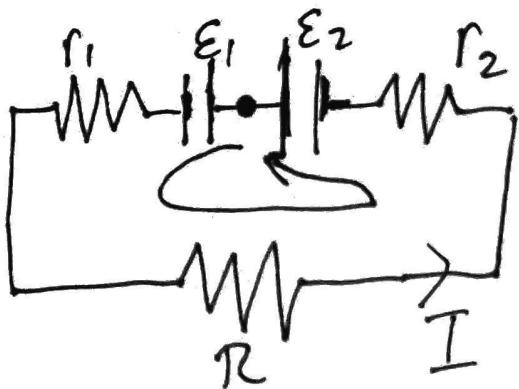
$$\boxed{\begin{aligned} I_1 &= 1 + I_2 = \frac{2}{3} \text{ A} \\ I_3 &= -I_2 = \frac{1}{3} \text{ A} \end{aligned}}$$




$$E_1 = 2 \text{ V}$$

$$E_2 = 6 \text{ V}$$

$$R_1 = 2 \Omega$$


$$R_2 = 4 \Omega$$

Junction rule:

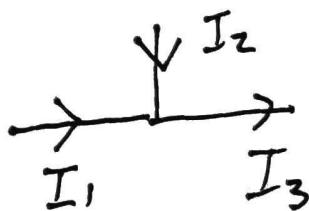


$$I_1 + I_2 = I_3$$

what they want:

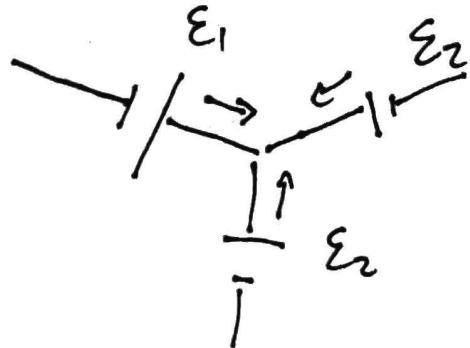


what
they
get:

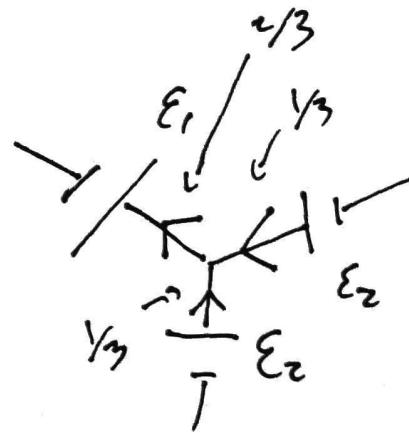

$$-I(r_1 + R + r_2) + \mathcal{E}_2 - \mathcal{E}_1 = 0$$



$$\Rightarrow I = \frac{\mathcal{E}_2 - \mathcal{E}_1}{r_1 + R + r_2}$$

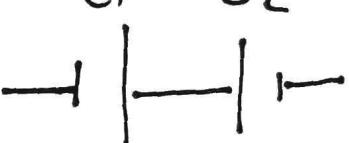Alternatively: $\mathcal{E}_1 \quad \mathcal{E}_2 \quad \mathcal{E}_2 - \mathcal{E}_1$



\approx $\mathcal{E}_2 - \mathcal{E}_1$

(Batteries in series)

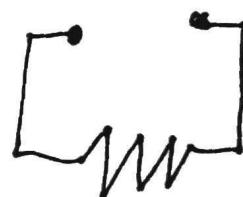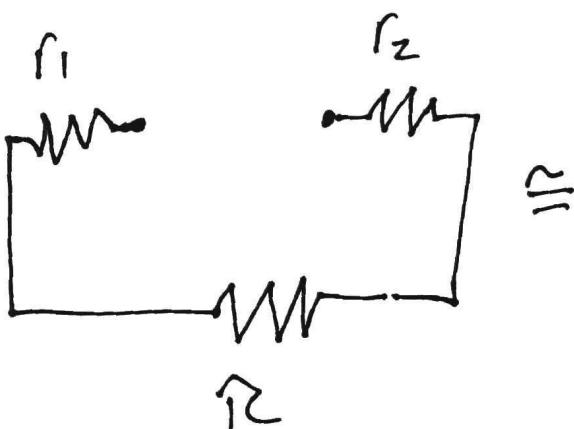


$$R_{\text{eff}} = r_1 + R + r_2$$

(Resistors in
series)

$$\Rightarrow I = \frac{\mathcal{E}_{\text{eff}}}{R_{\text{eff}}} = \frac{\mathcal{E}_2 - \mathcal{E}_1}{r_1 + R + r_2}$$

7]

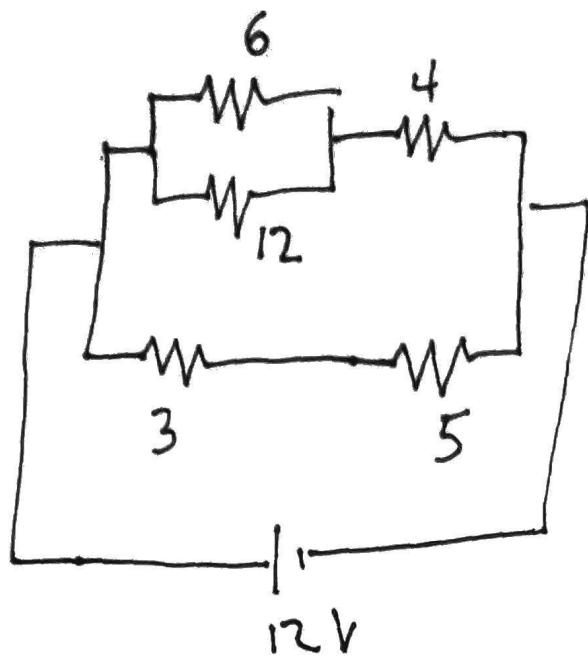


Find ΔV across
the 5Ω resistor.

(Use series and parallel rules:

$$\frac{R_1}{R_2} = \frac{R_{eq}}{R_1 + R_2}$$

$$\frac{R_1}{R_2} = \frac{R_{eq}}{R_1 + R_2}$$
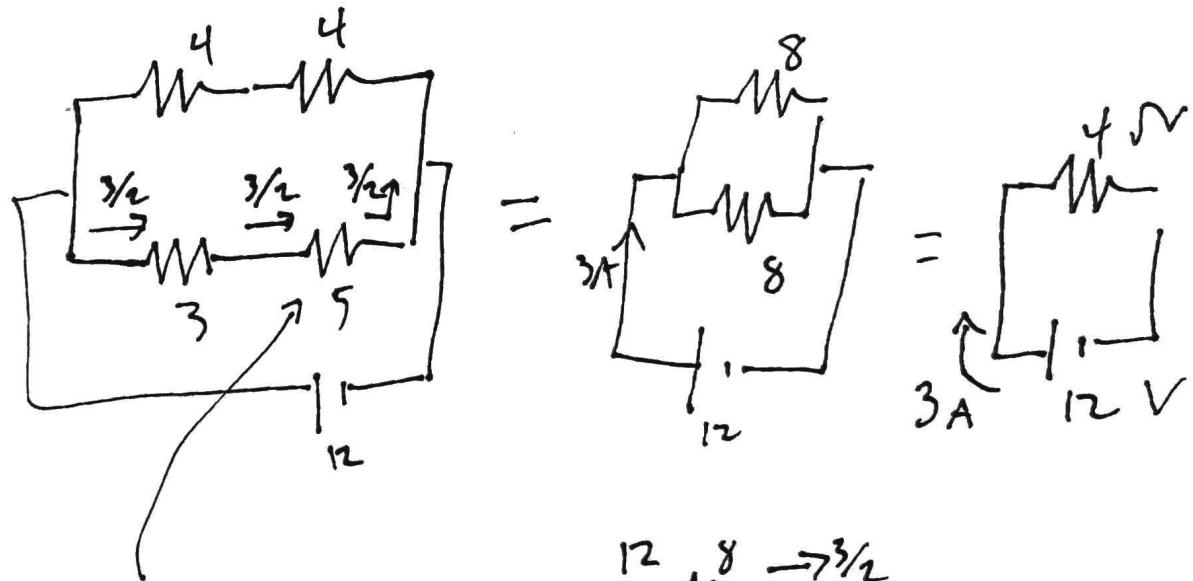
$$\frac{1}{6} + \frac{1}{12} = \frac{2}{12} + \frac{1}{12} = \frac{1}{4}$$



$$I = \frac{3}{2} A$$

$$\begin{aligned} V &= IR \\ &= 15/2 V \end{aligned}$$

